



Chapter 2

Digital Design Strategies and Techniques

Outline

- Design processing steps
- Analog building blocks for digital primitives
- Using a LUT to implement logic functions
- Discussion of design processing steps
- Synchronous logic rules
- Clocking strategies
- Logic minimization
- What does the synthesizer do ?
- Area/delay optimization

Design Processing Steps




- The processing steps from design to FPGA hardware
 - The design is *parsed for syntax errors*.
 - The design is *minimized and optimized* for the target architecture.
 - *Recognized structure elements* are replaced with selected library modules or cores.
 - *Timing and resource* requirements are estimated.
 - The design is converted to a *netlist*.
 - The design elements and modules are *linked* together and '*black-box*' modules are replaced with library or core module netlists.

Design Processing Steps

- The processing steps from design to FPGA hardware (cont.)
 - *Floorplanning* and *routing* attempts are made until the *timing* and *resource* constraints are met.
 - Timing and resource reports are extracted from the design. A *timing annotated netlist* is created to support post-routed simulation.
 - The *device configuration* files are created.

Analog Building Blocks for Digital Primitives

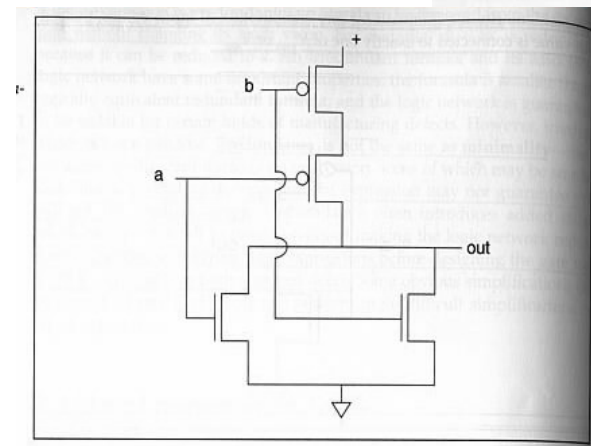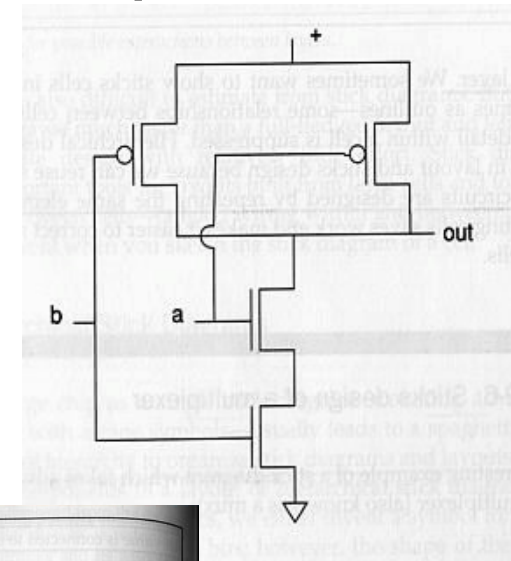 - Digital logics are implemented by
 - Transistors
 - Diodes
 - Resistors
- Examples
 - Inverter
 - Fig. 2-1
 - NAND gate
 - Fig. 2-2
 - NOR gate
 - Fig. 2-3



Using a LUT to Implement Logic Functions

- Most FPGAs use a multiplexer (MUX) Look-Up Table (LUT) as a basic logic element.
 - The LUT is versatile
 - Any function of the inputs is possible
 - The LUT is efficiently implemented in silicon
 - Configuration
 - MUX control inputs
 - Logic inputs
 - MUX data inputs
 - Be strapped to logic levels to implement the desired function

Using a LUT to Implement Logic Functions

- Example
 - An inverter implemented using MUX

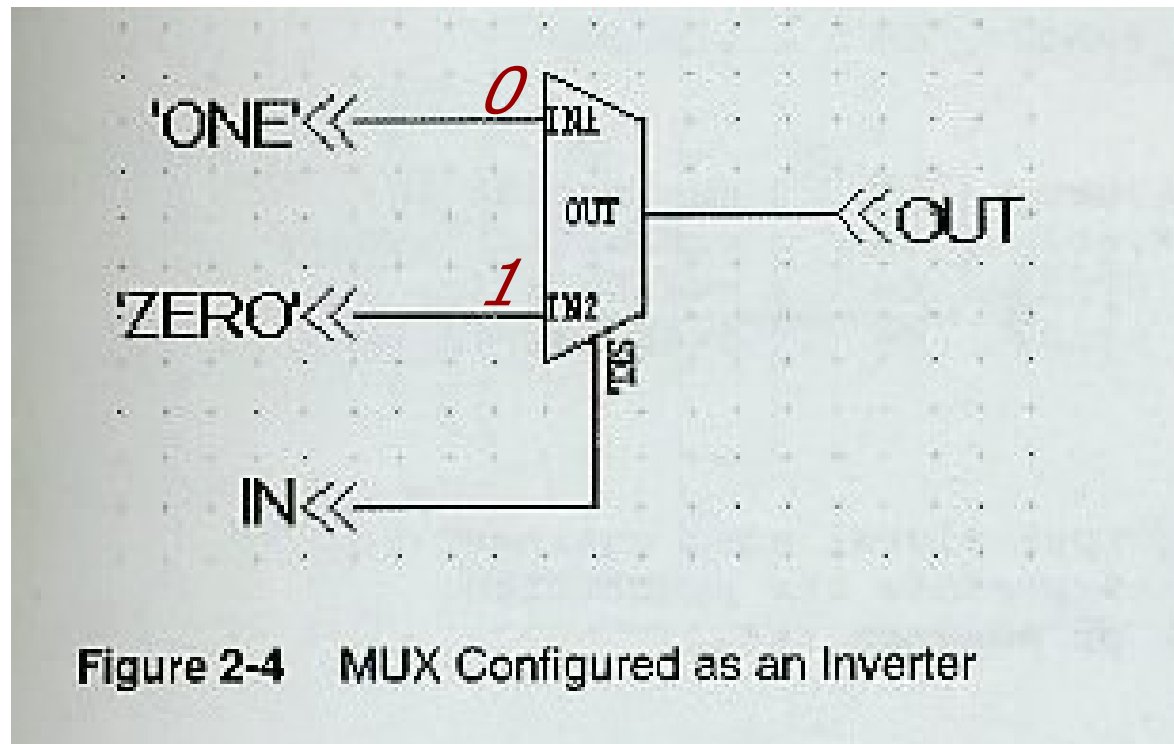


Figure 2-4 MUX Configured as an Inverter

Using a LUT to Implement Logic Functions

- Synthesis example
- Overheat detector

```
module overheat (clock, reset, overheat_in, pushbutton_in, overheat_out);
input          clock, reset, overheat_in, pushbutton_in;
output        overheat_out;
reg           overheat_out;
reg           pushbutton_sync1, pushbutton_sync2;
reg           overheat_in_sync1, overheat_in_sync2;

// Always synchronize inputs that are not phase related to
// the system clock.
// Use double-synchronizing flipflops for external signals
// to minimize metastability problems.
// Even better would be some type of filtering and latching
// for poorly behaving external signals that will bounce
// and have slow rise/fall times.

always @ (posedge clock or posedge reset)
begin
    if (reset)
        begin
            pushbutton_sync1 <= 1'b0;
            pushbutton_sync2 <= 1'b0;
            overheat_in_sync1 <= 1'b0;
            overheat_in_sync2 <= 1'b0;
        end
    else
        begin
            pushbutton_sync1 <= pushbutton_in;
            pushbutton_sync2 <= pushbutton_sync1;
            overheat_in_sync1 <= overheat_in;
            overheat_in_sync2 <= overheat_in_sync1;
        end
end

// Latch the overheat output signal when overheat is
// asserted and the user presses the pushbutton.
always @ (posedge clock or posedge reset)
begin
    if (reset)
        overheat_out <= 1'b0;
    else if (overheat_in_sync2 && pushbutton_sync2);
        overheat_out <= 1'b1;
    end
end

endmodule
```


Using a LUT to Implement Logic Functions

- Graphical version of the netlist

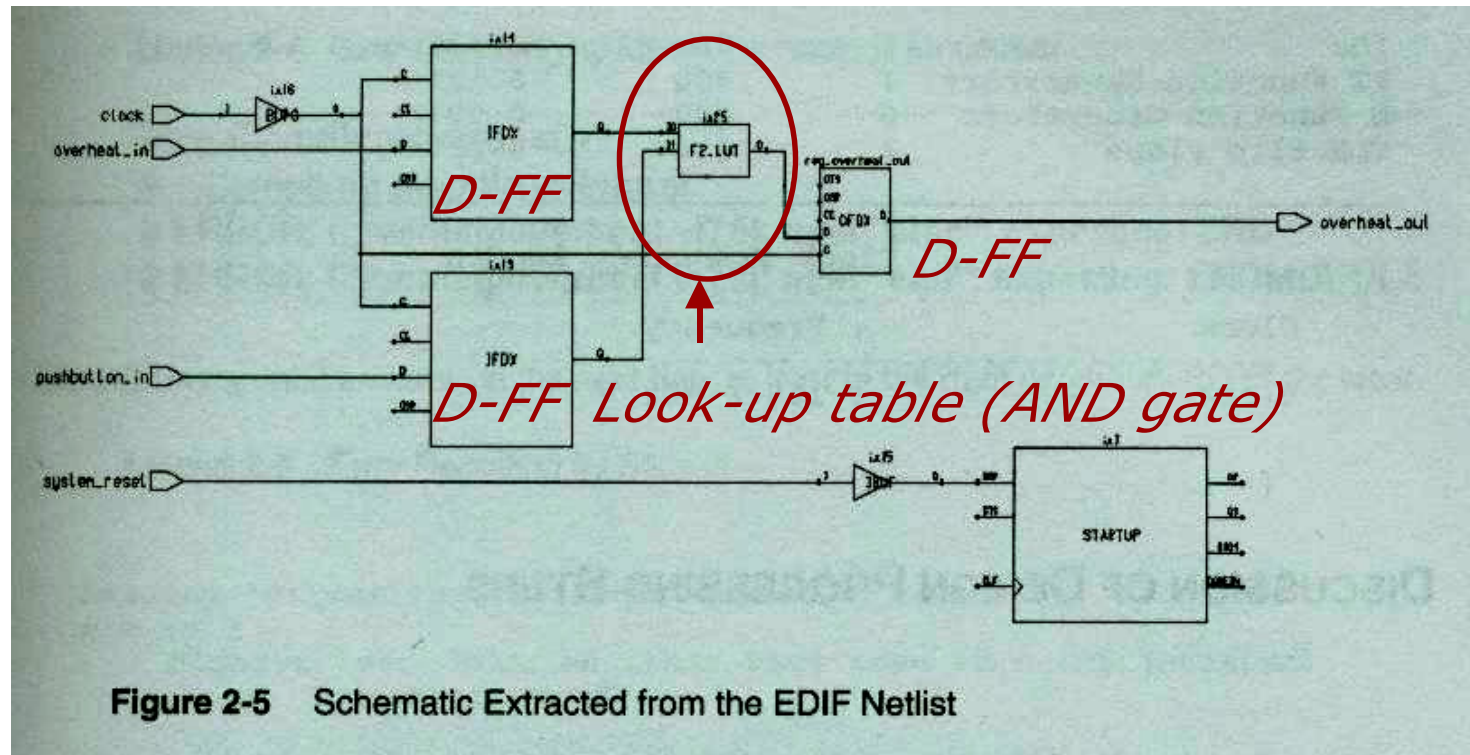


Figure 2-5 Schematic Extracted from the EDIF Netlist

Using a LUT to Implement Logic Functions

- Graphical version of the netlist
 - Notes
 - The correct use of *global* resources for *clock* and *reset*
 - Using a *LUT for AND gate* that is located between two DFF's
 - Verilog does not support direct assignment of hardware resources
 - It is the designer's job to assure that these inferences are made correctly.

Using a LUT to Implement Logic Functions

- Estimation of the timing and resource requirements

```
*****
```

```
Cell: overhear View: INTERFACE Library: work
```

```
*****
```

```
Number of ports : 5
Number of nets : 13
Number of instances : 10
Number of references to this view : 0
```

```
IOs 5 77 6.49%
FG Function Generators 1 800 0.13%
H Function Generators 0 400 0.00%
CLB Flip Flops 2 800 0.25%
```

Resource information

```
Total accumulated area :
```

```
Number of BUFG : 1
Number of CLB Flip Flops : 2
Number of FG Function Generators : 1
Number of IBUF : 1
Number of IOB Input Flip Flops : 2
Number of IOB Output Flip Flops : 1
Number of Packed CLBs : 1
Number of STARTUP : 1
```

```
Clock Frequency Report
```

```
Clock : Frequency
-----
clock : 118.8 MHz
```

Timing information

```
*****
```

```
Device Utilization for 4010x1PQ100
```

```
*****
```

```
Resource Used Avail Utilization
```

```
-----
```

Discussion of Design Processing Steps


- Syntax checking
 - Identifying the syntax, typing, and other errors
 - Where is the error ?
 - A semicolon is appended on one of the *if* statement (*Listing 2-3, p. 48*)
 - Different tools give different error messages
 - It makes good sense to have several tools available for checking your code.

Discussion of Design Processing Steps

- Design minimization and optimization
 - Hardware configuration
 - FPGA
 - Semi-custom FPGA
 - ASIC
 - The synthesis result is related to the logic structure of FPGA

Discussion of Design Processing Steps

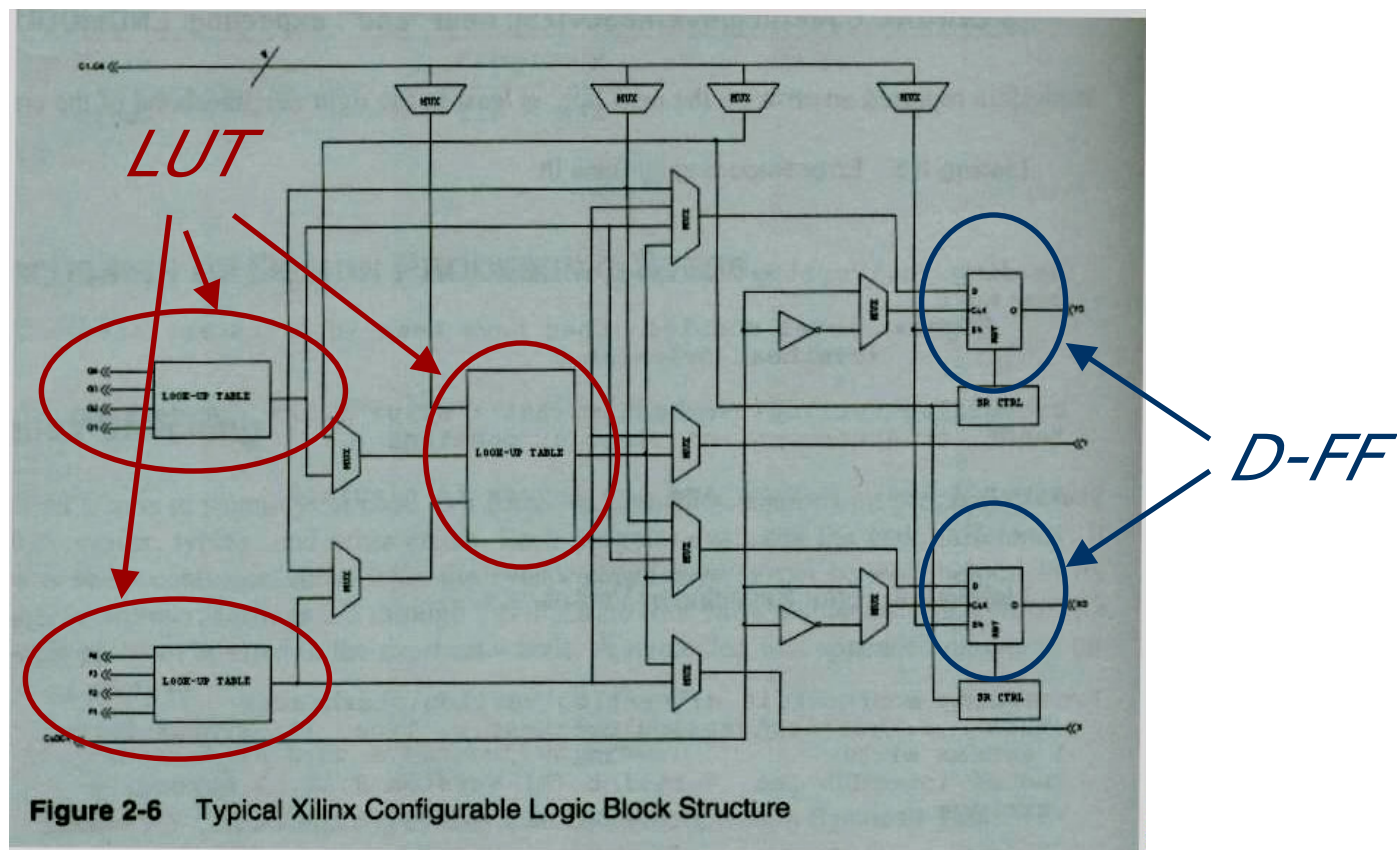- Xilinx 4K family Configuration Logic Block (CLB)
 - Two 4-input LUTs feeding a pair of flipflops



Discussion of Design Processing Steps

- Synthesis process steps

- *Step 1*

- *Flattening* the design into *large Boolean equations* with *one equation* for each module output, design section output, or register output

Discussion of Design Processing Steps

■ Example

■ A simple 2-bit adder code

```
module adder (clock, reset, a, b, c); // Simple adder (no carry input).
    input    clock, reset, a, b;
    output   c;
    reg     [1:0]    c;
    always @ (posedge clock or posedge reset)
    begin    if (reset)
                c = 2'b0;
            else
                c = a + b;           // Adder.
            end
endmodule
```

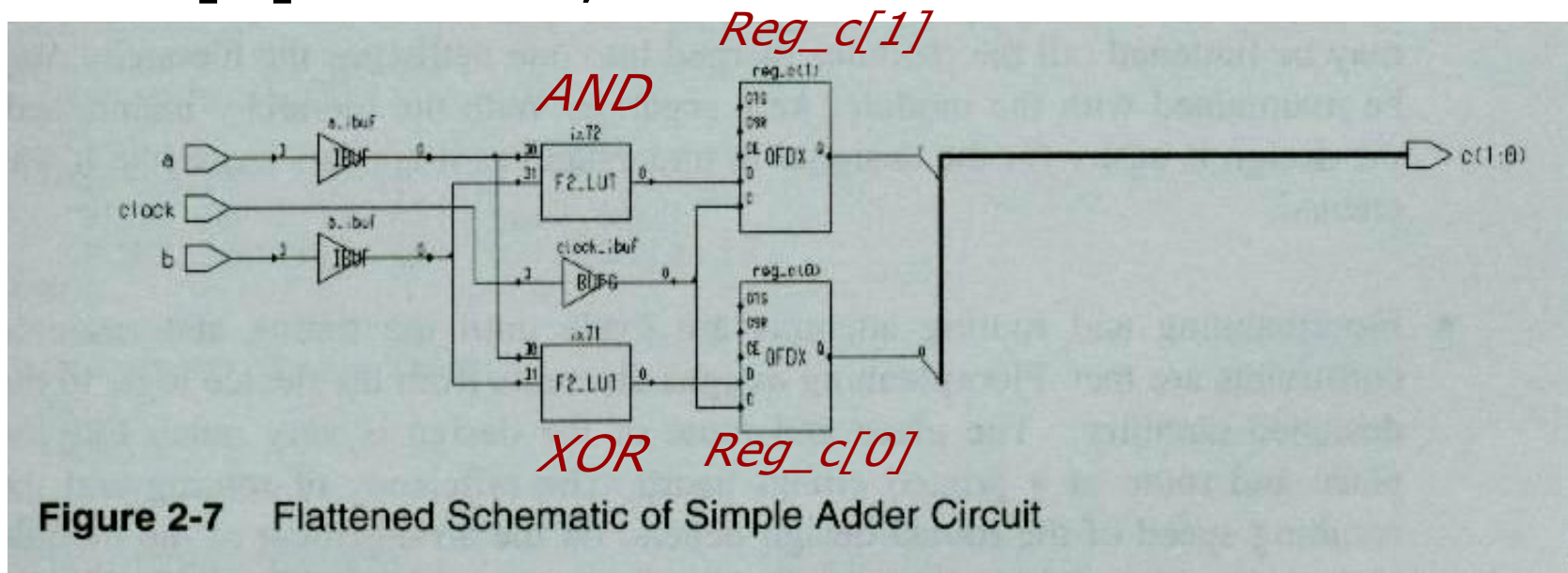

Discussion of Design Processing Steps

- *Truth table* for simple adder example
 - C[0] could be represented by an XOR gate
 - C[1] could be represented by an AND gate

a	b	C[1]	C[0]
0	0	0	0
0	1	0	1
1	0	0	1
1	1	1	0

Discussion of Design Processing Steps

- A flattened version of the simple adder example
 - $C[0] \leq a \wedge b$;
 - $C[1] \leq a \oplus b$;



Discussion of Design Processing Steps

■ Synthesis process steps

■ *Step 2*

- *Minimizing the Boolean equations*
 - By recognizing and removing redundant logic terms

■ *Step 3*

- Recognized structure elements are replaced with selected modules.
 - E.g. $a \leq a-1 \rightarrow$ Down counter
 - Replacing the logic with a pre-defined circuit optimized for the target architecture for either speed or area

Discussion of Design Processing Steps

■ Synthesis process steps

■ *Step 4*

- *Timing and resource* requirements are *estimated* by the compiler
 - *May not be accurate enough*
 - *Why the estimation is not accurate ?*
 - The manufacturer may have made *changes* to the timing parameters.
 - The *library* and *black-boxes* are *not* yet part of the design netlist.

■ *Step 5*

- The design is converted to a netlist
 - The most common one is EDIF format

Discussion of Design Processing Steps

- Synthesis process steps

- *Step 6*

- The design elements and modules are *linked* together and '*black-box*' modules are replaced with library module netlists.

Discussion of Design Processing Steps

■ Synthesis process steps

■ *Step 7*

- *Floorplanning* and *routing* attempts are made until the *timing* and *resource* constraints are met.
 - Floorplanning assigns elements from device logic to the designed circuitry.
 - The efficiency of routing and the resulting speed of the routed design depend on the *arrangement of the module element*.
- Typical routing densities of FPGAs
 - Altera → *65%*
 - Xilinx → *85%*
 - *Capability of 100% routing of all logic is only an advertisement.*

Discussion of Design Processing Steps

■ Synthesis process steps

■ *Step 8*

- Timing and resource reports are extracted from the design. A *timing annotated netlist* is created to support post-routed simulation
 - A common format is SDF format
 - SDF → Standard Delay Format
 - Example
 - Listing 2-9

Discussion of Design Processing Steps

■ Synthesis process steps (SDF netlist)

Listing 2-9 Example of an SDF Netlist

```
(DELAYFILE
(SDFVERSION "2.0")
(DESIGN "adder")
(DATE "08/31/99 09:21:34")
(VENDOR "Exemplar Logic, Inc., Alameda")
(PROGRAM "LeonardoSpectrum Level 3")
(VERSION "v1999.1d")
(DIVIDER /)
(VOLTAGE)
(PROCESS)
(TEMPERATURE)
(TIMESCALE 1 ns)
(CELL
(CELLTYPE "F2_LUT")
(INSTANCE ix72)
(DELAY
(ABSOLUTE
(PORT IO (::3.25) (::3.25))
(PORT I1 (::3.25) (::3.25))))))
(CELL
(CELLTYPE "F2_LUT")
(INSTANCE ix71)
(DELAY
(ABSOLUTE
(PORT IO (::3.25) (::3.25))
(PORT I1 (::3.25) (::3.25))))))
(CELL
(CELLTYPE "BUFG")
(INSTANCE clock_ibuf)
(DELAY
(ABSOLUTE
(PORT I (::0.00) (::0.00))))))
(CELL
(CELLTYPE "OFDX")
(INSTANCE reg_c_1)
(DELAY
(ABSOLUTE
(PORT C (::3.25) (::3.25))
(PORT D (::2.77) (::2.77))))))
(CELL
(CELLTYPE "OFDX")
(INSTANCE reg_c_0)
(DELAY
(ABSOLUTE
(PORT C (::3.25) (::3.25))
(PORT D (::2.77) (::2.77))))))
(CELL
(CELLTYPE "IBUF")
(INSTANCE reset_ibuf)
(DELAY
(ABSOLUTE
(PORT I (::2.77) (::2.77))))))
(CELL
(CELLTYPE "IBUF")
(INSTANCE a_ibuf)
(DELAY
(ABSOLUTE
(PORT I (::2.77) (::2.77))))))
(CELL
(CELLTYPE "IBUF")
(INSTANCE b_ibuf)
(DELAY
(ABSOLUTE
(PORT I (::2.77) (::2.77))))))
(CELL
(CELLTYPE "STARTUP")
(INSTANCE ix56)
(DELAY
(ABSOLUTE
(PORT GSR (::2.77) (::2.77))))))
)
```


Discussion of Design Processing Steps


- Synthesis process steps
 - *Step 9*
 - The *device configuration* files are created.
 - Way of programming
 - EPROM programming
 - Downloading through serial or parallel cable
 - Stored in memory
 - Programming devices
 - Micro-processors
 - Stand-alone programmer
 - Device types
 - ISP (In-System Programming) type
 - Re-programmable type

Discussion of Design Processing Steps

■ Shifty (詭詐的) logic circuits

■ Example 1

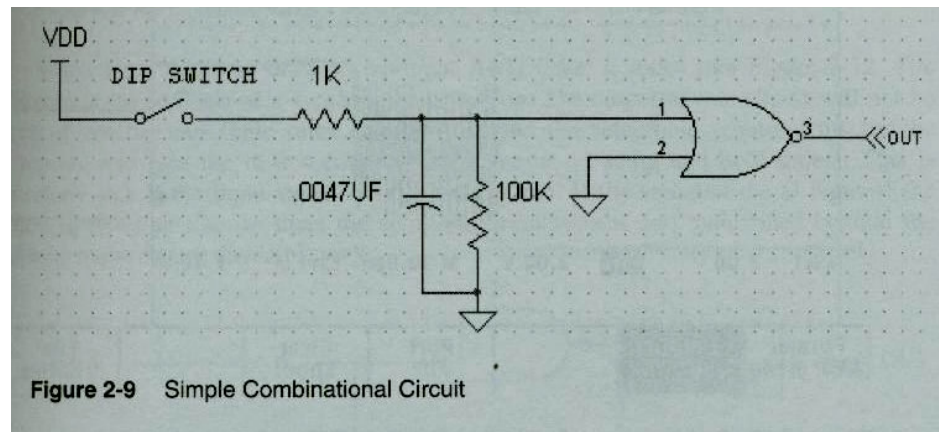- 2-input NOR gate
 - Seems shifty or flaky (言里言怪的)
 - The output is very likely to be glitchy when the inputs change.
 - Source for glitches → *Switch bounces*




Discussion of Design Processing Steps

- Oscilloscope trace of 2-input NOR
 - Switch bounce occurs in DIP switch
 - To use feedback (hysteresis) to filter switch bounce

Node 3

Node 1

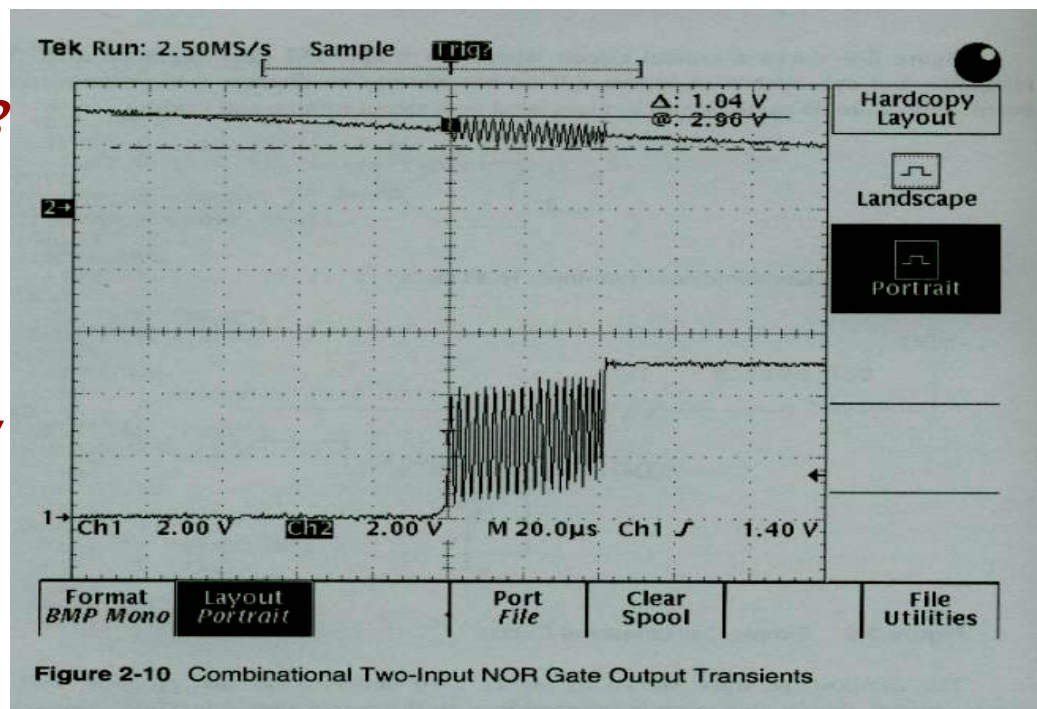

Discussion of Design Processing Steps

- Another source for glitches
 - *RC time delay* causing signals traveling with different arrival time
 - R represents
 - The sum of source and routing impedance
 - C represents
 - The net loading
 - Could be controlled by setting fanout constraint in synthesis
 - Example 2
 - 2-input AND gate with RC network

Discussion of Design Processing Steps

- Combinational AND gate


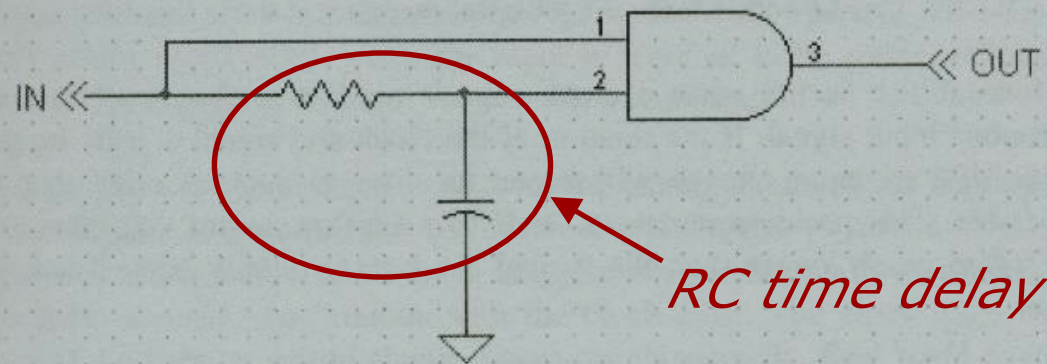


Figure 2-11 Combinational Two-Input AND Gate with RC Network

Discussion of Design Processing Steps

■ Solution

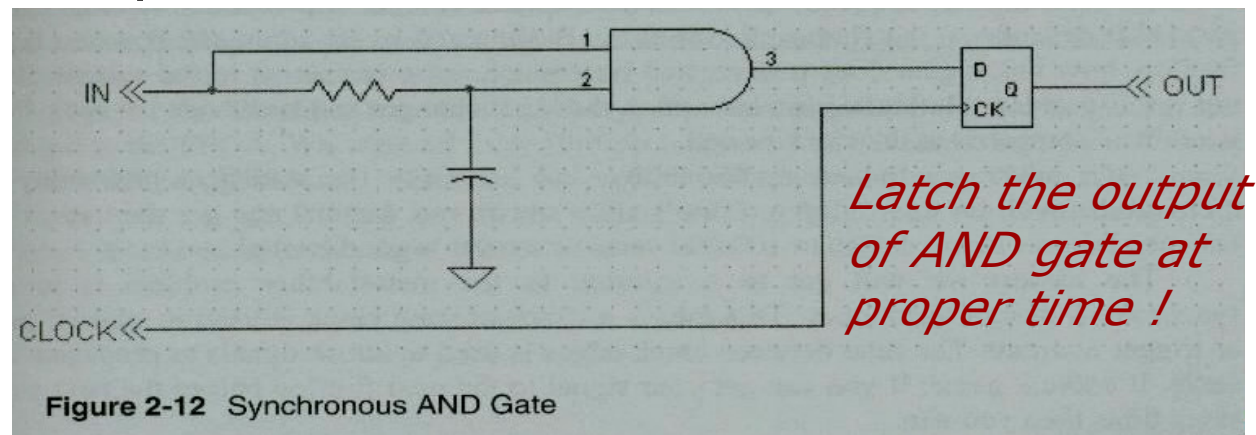
- Synchronous AND gate
- Adding a D-FF in the output node to remove the glitches by meeting
 - Synchronous logic rules
 - Setup and hold times of the D-FF



Synchronous Logic Rules

■ Metastability

 - Occurs when a *clock edge* is *random* with respect to a change of an *asynchronous input*
- The FF output may take a longer time than typical clock-to-Q delay of FF data sheet




Synchronous Logic Rules

- Solution to the metastability
 - Using *synchronous design technique*
 - Adopting a synchronizing clock to qualify, gate, or trigger a circuit
 - The time between clock edges (clock period) is used to allow signals to propagate and settle
 - *Narrowing the metastability window*
 - Narrowing the setup-and-hold time period by *increasing the speed of FF*

Synchronous Logic Rules

 - Setup and hold times
 - The inputs must *meet the setup and hold times* so that the output of FFs is not metastable (can be predictable).
 - The input changes in T_{su} earlier than the synchronizing clock edge
 - The input is required to be stable in T_h later than the synchronizing clock edge




Synchronous Logic Rules

- *Where* do the setup and hold times occur ?
 - *Coming from the analog nature of the flipflop design*
 - The flipflops use *feedback* implemented with cross coupled gates to hold a state.
 - It *takes time* for the FF to achieve their stable state.

Synchronous Logic Rules

 - Real World design
 - Real World clock has *rise/fall times*
 - *Do not change abruptly*



- FF requires *stable inputs during setup/hold time*

Synchronous Logic Rules

- Asynchronous input problem

- When an *asynchronous input* drives *multiple flipflops*, and the input *changes near the clock edge*, some flipflops outputs *will* change and some *will not*.

- *RC delay* is caused by the FPGA routing and loads

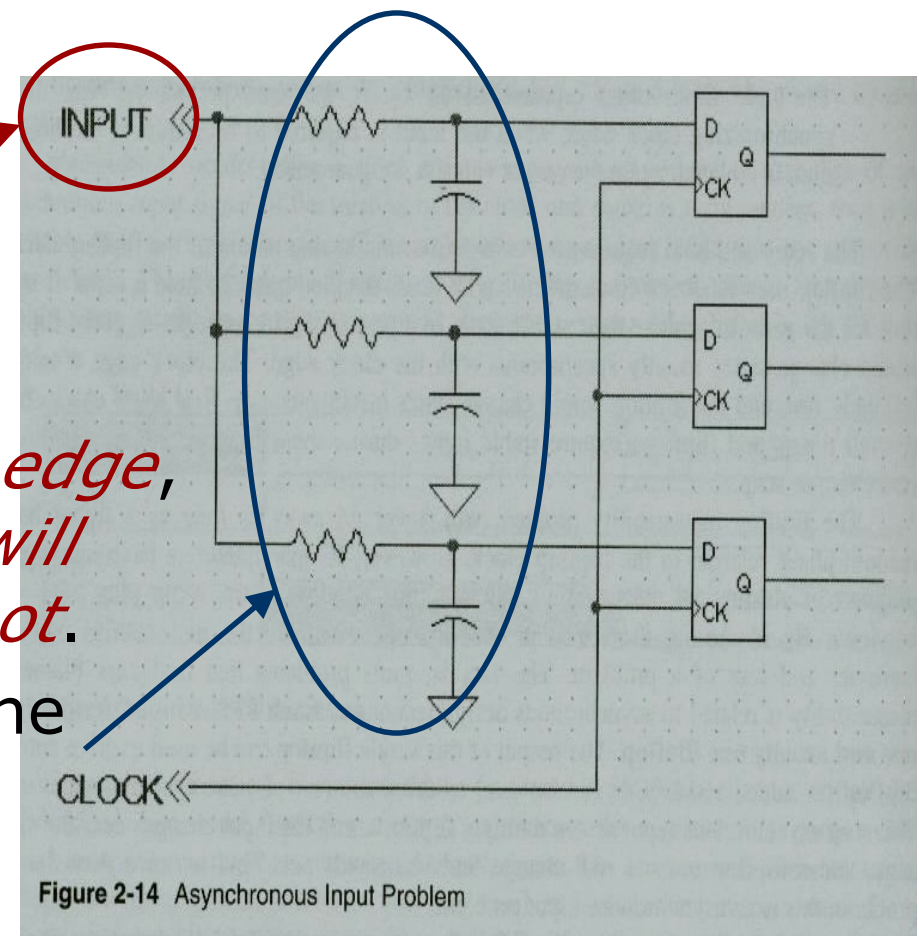



Figure 2-14 Asynchronous Input Problem

Synchronous Logic Rules

- Solution to the asynchronous input problem
 - *Synchronizing* the input with a *single* flipflop
 - *Do not violate* the setup/hold time requirement


Synchronous Logic Rules

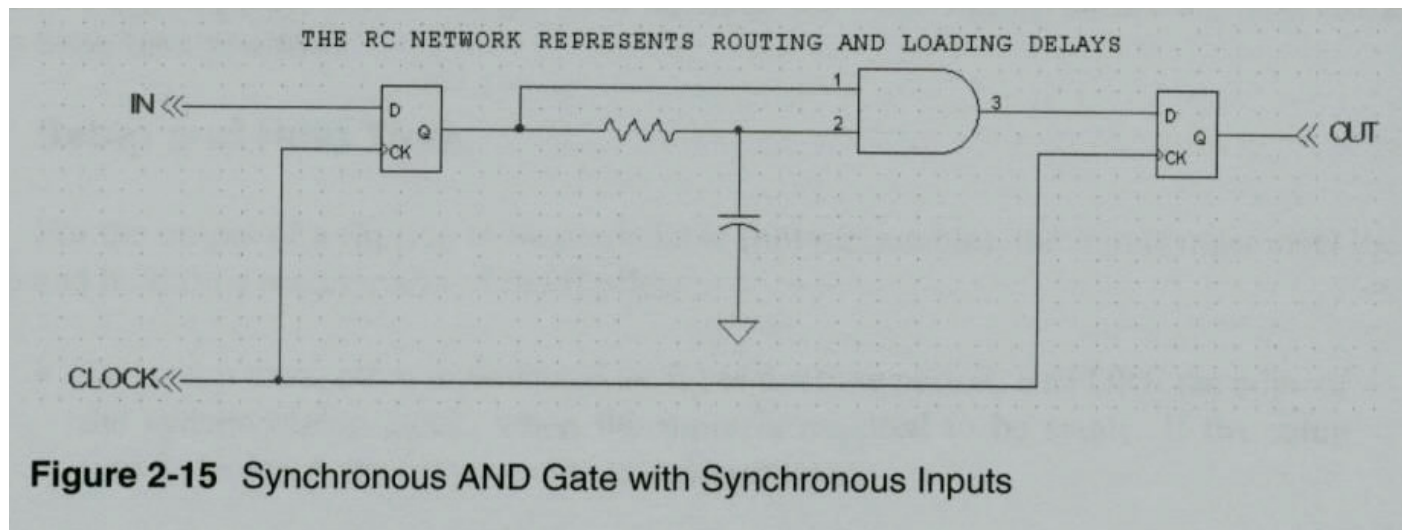- How can I create a nearly trouble-free design ?
 - Always synchronize your inputs !
 - An *asynchronous input* drives *exactly one* FF.
 - The *output of this FF* can be *safely* used to drive the rest of your *synchronous circuitry*.



Synchronous Logic Rules

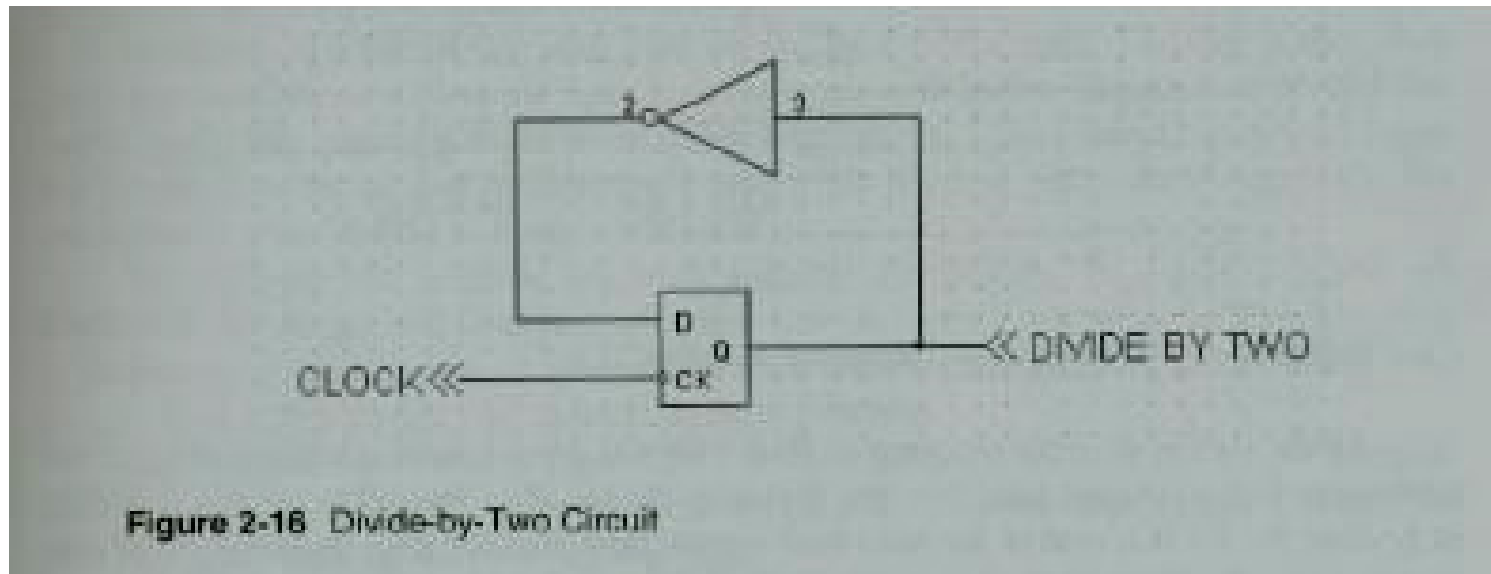- Estimating the max. clock frequency
 - Example: divided-by-two circuit




Synchronous Logic Rules

- D-FF specifications
 - FF minimum input set-up time
 - $T_{su}=1ns$
 - FF minimum input hold time
 - $T_h=1ns$
 - Maximum clock-to-output delay
 - $T_{co}=1ns$
 - Maximum propagation delay (Q to D)
 - $T_{qd}=1ns$

Synchronous Logic Rules

- Timing calculation

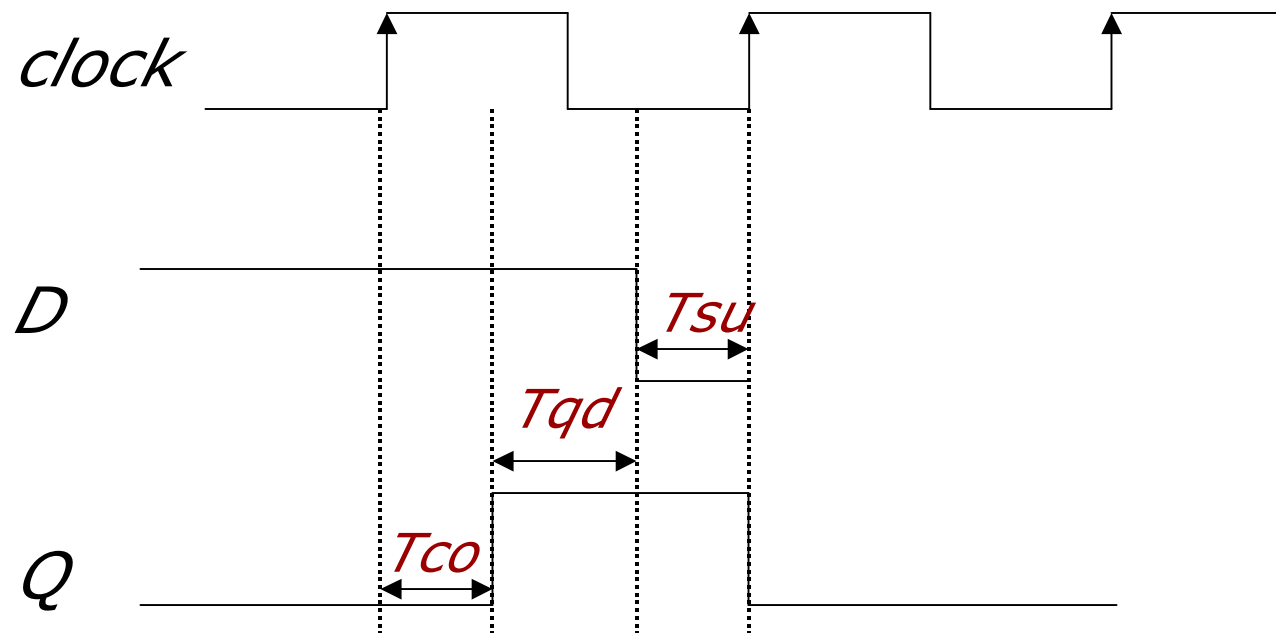

Minimum clock period = 3ns \rightarrow Max clock freq = 333.33MHz

Synchronous Logic Rules

- Cascaded FF v.s. Timing delay
 - How can this circuit work reliably ?(Fig.2-17)
 - What if the min. clock-to-output delay of U1 is less then the hold time requirement of U2 ?
 - *U2 will directly latch the updated value instead of the old value of U1 !!!*
 - *This is not what we want !!!*
 - *FPGA chip designer will create a logic cell that assure the circuit will work !!!*

Synchronous Logic Rules


- Clock skew problem
 - Example: two FFs connected in series with clock skew (Fig. 2-19)
 - What is the problem ?
 - *The clock skew will cause the U2 always latches the newest value instead of the old value from U1 !*
 - *Or U2 may latch the unknown value due to the violation of input set-up time caused by the clock skew !*

Synchronous Logic Rules

- What is the solution ?
 - *Minimizing the clock skew situation*
 - FPGA
 - The FPGA chip designer has provided low-skew clock network to assure that the *longest skew of the clock* anywhere across the device *is shorter than* the shortest sum of clock-to-Q and signal routing propagation delay.
 - ASIC
 - H-tree (or balanced) clock distribution network to reduce the clock skew situation

Synchronous Logic Rules

- H-tree clock distribution

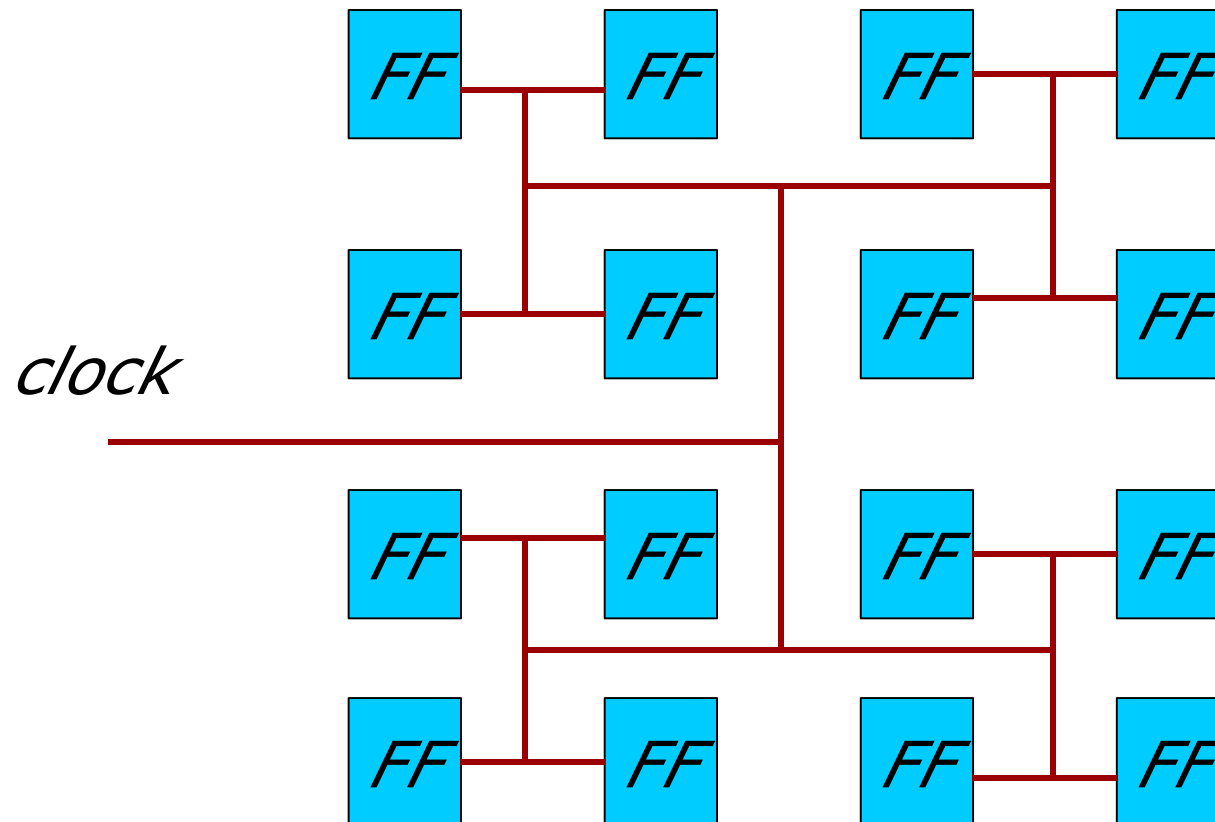

Clocking Strategies

- The most important decision the FPGA designer makes is
 - Clocking strategies
 - This must be considered carefully.
 - An error in clocking can doom a design.

Clocking Strategies

- Suggested clocking strategies (1)
 - When designing an ASIC, if power consumption is **NOT** an issue,
 - Use one master clock on all FFs
 - Replace lower-frequency clocks with clock enables
 - The design has one clock, which results in the simplest timing analysis.

Clocking Strategies

- Suggested clocking strategies (2)
 - When designing an ASIC, if power consumption **IS** an issue,
 - Running FFs in lower clock frequency in selected parts of the design is OK.
 - Make the design smaller and/or reduce the clock frequency to reduce the power consumption.
 - Minimizing the amount of circuitry running at high speed.
 - Be forced to deal with the problem of synchronizing signals crossing clock domains in exchange for reduced power consumption.

Clocking Strategies

- Suggested clocking strategies (3)
 - When designing an ASIC, but using FPGAs as prototypes,
 - *For fast FPGAs (ASIC-like)*
 - Running the design with one master clock
 - *For slow FPGAs (SRAM-based devices)*
 - Will probably be forced to run modules at the lowest possible speed to get the design work.
 - Drive FFs with multiple clocks,
 - Creating clocks in a central clock generator module,
 - Minimizing the interconnection between clock domains,
 - Making sure signals that cross clock domains are properly synchronized.

Clocking Strategies

- Suggested clocking strategies (4)
 - When doing a *fast* FPGA design,
 - Use up the global clock resources
 - Partitioning the design to minimize signals crossing clock domains
 - Synchronizing the signals properly.
 - When doing a *slow* FPGA design,
 - Either strategy is fine.

Clocking Strategies

- Clock enable
 - Verilog HDL *does not* support dedicated clock enable signals.
 - FPGA synthesis vendors *may provide* this support through compiler directives.
 - The code in Listing 2-10 may be synthesized into *different ways* depending on the targeted FPGA.

Clocking Strategies

- Clock-Enable example (Listing 2-10)

```
module clock_en(out, in, clock, clock_enable1, clock_enable2, reset);  
  
output out;  
input in, clock, clock_enable1, clock_enable2, reset;  
reg out;  
  
always @ (posedge clock or posedge reset)  
begin  
if (reset)  
    out<=0;  
else if (clock_enable1)  
    out<=out; // Hold output if not enabled.  
else  
    out<=(in & clock_enable2);  
end  
endmodule
```

Clocking Strategies

- Synthesized clock enable
 - Fig. 2-22

Clocking Strategies

- In synthesis, the synthesizer may insert *added logic* into the clock-enable path.
 - Fig. 2-23

Clocking Strategies

- The clock enable implementation in a technology that *does not have a clock-enable feature in its logic block.*
 - Fig. 2-24

Logic Minimization

- A synthesizer can recognize and remove redundant logic.
 - Listing 2-11 v.s. Listing 2-12

Listing 2-11

```
input    test1, test2, test3;  
output  sample;
```

```
sample = ((test1 & test2 & test3) | (test1 & !test2 & test3)  
          | (test1 & test2 & !test3));
```

Listing 2-12

```
input    test1, test2, test3;  
output  sample;
```

```
sample = ((test1 & (test2 | test3)));
```

Using K-map



The compiler can also recognize equivalent logic equations

Logic Minimization

- The synthesizer will not be able to extract the redundant logic if the logic is spread over across register boundaries.
 - Fig. 2-26

Logic Minimization

- How can we take advantages of the synthesis tool's capability to minimize the logic ?
 - *Never create purely combinational modules !!!*
 - *None of the popular FPGA architectures have purely combinational logic elements.*
 - *Mixing the combinational logic with the synchronous logic to allow the synthesis tool to merge the logic into the resources available in the device.*

Logic Minimization

- Combinational logic clouds feeding flipflops
 - Fig. 2-27

What does the synthesizer do ?

- Synthesizer's role
 - Take Verilog HDL and maps it into hardware
 - Procedures
 - *Minimize logic equations* by removing redundant logic terms
 - *Map the resulting Boolean equations onto the available hardware elements in FPGAs*
 - Example
 - 7-segment decoder

What does the synthesizer do ?

- Truth table for 7-segment decoder

<i>BCD input</i>				<i>Segment output</i>						
<i>B3</i>	<i>B2</i>	<i>B1</i>	<i>B0</i>	<i>a</i>	<i>b</i>	<i>c</i>	<i>d</i>	<i>e</i>	<i>f</i>	<i>g</i>
0	0	0	0	1	1	1	1	1	1	0
0	0	0	1	0	1	1	0	0	0	0
0	0	1	0	1	1	0	1	1	0	1
0	0	1	1	1	1	1	1	0	0	1
0	1	0	0	0	1	1	0	0	1	1
0	1	0	1	1	0	1	1	0	1	1
0	1	1	0	1	0	1	1	1	1	1
0	1	1	1	1	1	1	0	0	0	0
1	0	0	0	1	1	1	1	1	1	1
1	0	0	1	1	1	1	1	0	1	1

What does the synthesizer do ?

- Let us consider the output of “a” segment

- The reduced equation for “a” segment

What does the synthesizer do ?

- Verilog design for 7-segment display decoder “a” term

```
module seven_seg (clk, reset, bcd_input, a_segment);  
  
input                clk, reset;  
input [3:0]         bcd_input;  
output              a_segment;  
reg                  a_segment;  
  
always @ (posedge clk or posedge reset)  
    if (reset)  
        a_segment<=0;  
    else  
        begin case (bcd_input)  
            {1'b0, 1'b0, 1'b0, 1'b0}: a_segment <= 1'b1;  
            {1'b0, 1'b0, 1'b0, 1'b1}: a_segment <= 1'b0;  
            {1'b0, 1'b0, 1'b1, 1'b0}: a_segment <= 1'b1;  
            {1'b0, 1'b0, 1'b1, 1'b1}: a_segment <= 1'b1;  
            {1'b0, 1'b1, 1'b0, 1'b0}: a_segment <= 1'b0;  
            {1'b0, 1'b1, 1'b0, 1'b1}: a_segment <= 1'b1;  
            {1'b0, 1'b1, 1'b1, 1'b0}: a_segment <= 1'b1;  
            {1'b0, 1'b1, 1'b1, 1'b1}: a_segment <= 1'b1;  
            {1'b1, 1'b0, 1'b0, 1'b0}: a_segment <= 1'b1;  
            {1'b1, 1'b0, 1'b0, 1'b1}: a_segment <= 1'b1;  
            default: a_segment <= 0;  
        endcase  
    end  
endmodule
```

What does the synthesizer do ?

- Synthesized Logic for 7-segment display decoder “a” term
 - Fig. 2-28

Area/Delay Optimization

- Two fundamental concerns in implementing a design
 - How big is it ?
 - How fast will it operate ?
- The goal of our quest is to achieve *good enough*
 - To meet system requirements like
 - Product cost
 - Development cost
 - Performance
 - Reliability
 - Maintainability
 - Time to market

Area/Delay Optimization

- *The experienced designer always leaves a way out of a problem by insuring that a faster or denser device, if at all possible, is available in the same device footprint.*
 - *Instead of redesigning a circuit board to accommodate a new device at great expenses.*