

## Department of Computing Course 112 - Hardware Tutorial 7

This tutorial contains exercises that are assessed. Make certain that your name, initials and group are clearly filled in. Do all your work on this sheet and hand it in at the end of the tutorial session.


LAST NAME \_\_\_\_\_ INITIALS \_\_\_\_\_ GROUP \_\_\_\_\_

Small calculators work with **BCD** (binary-coded-decimal) digits. This means that four bits represent decimal digits **0** to **9** and thus six combinations of the four bits are not used. A common bit assignment for **BCD** digits are:

Bits	0000	0001	0010	0011	0100	0101	0110	0111	1000	1001
Digit	0	1	2	3	4	5	6	7	8	9

Bits	1010	1011	1100	1101	1110	1111
Digit	-	-	-	-	-	-

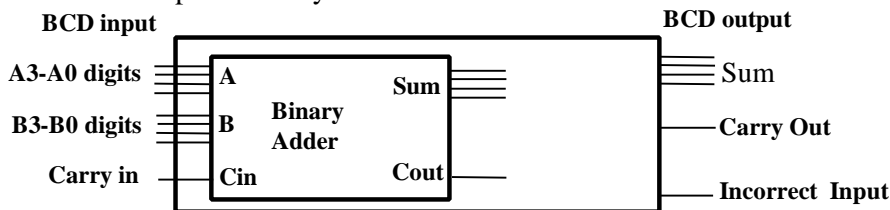In preparation for the design of a calculator, we want to build an **adder of two BCD digits**, which will be made up of a binary adder and some extra circuits.




First, we need to design a circuit that recognises incorrect **BCD** input digits.

### Problem 1

Design and draw the minimised circuit for the "**incorrect BCD digit**" signal generator. First draw the Karnaugh map and determine the minimised boolean equation, then draw the actual circuit.

		Q1		Q0	
		00	01	11	10
Q3Q2	00				
	01				
	11				
	10				

Incorrect BCD digit =

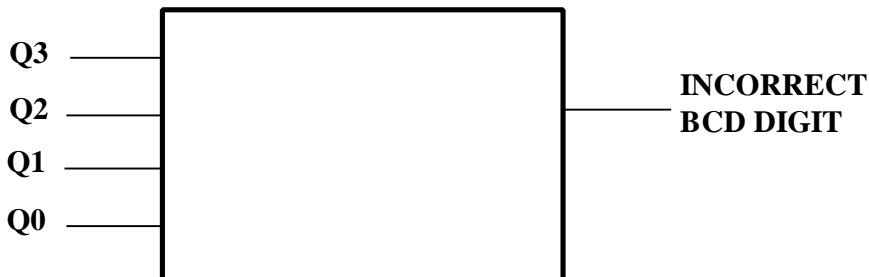


Two of the circuits of problem 1, and a two-input **OR** gate will be needed to provide an **Incorrect Input** signal which indicates that either or both input digits are made up of invalid bit combinations. We now plan to use a four-bit binary adder to provide the sum of two BCD digits.

**Problem 2.** Design the **BCD Carry Out**

For a sum of less than **9** the **Carry Out** signal should have a **0** value. For larger sums it should be **1**, equivalent to carry 10. For example two **BCD** digits, say **5** and **8** should produce **3** for the **BCD** output and a **Carry Out** of **1**, read as **13**. However the binary adder carry does not do this. The possibilities generating a carry are summarised by the following table.

Sum	10	11	12	13	14	15	16	17	18	19
Binary Sum	1010	1011	1100	1101	1110	1111	0000	0001	0010	0011
Binary Cout	0	0	0	0	0	0	1	1	1	1
BCD Sum	0000	0001	0010	0011	0100	0101	0110	0111	1000	1001
BCD Cout	1	1	1	1	1	1	1	1	1	1

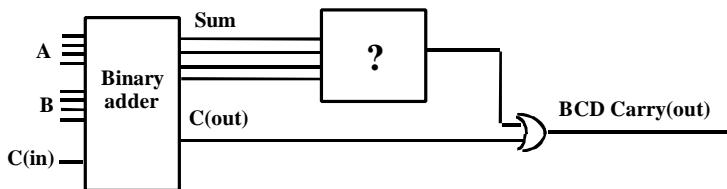An ingenious classmate of yours comes up with the following scheme for the **BCD Carry Out** generator:



**It works!** Find the combinational circuit (shown with the question mark above) that will make it work:

		Q1 Q0			
		00	01	11	10
Q3Q2	00				
	01				
	11				
	10				

**BCD Carry =**

**Problem 3.**

Only the binary sum of the two BCD digits has been generated so far. The same ingenious classmate of yours has a solution for generating the correct **BCD** output sum as well. All you have to do (she says) is to use another binary adder to fix up the output when a BCD carry is generated. What should the circuit (? on the diagram below) be? (**Hint:** The results will be simpler than you think!)

